

Indian Institute of Information Technology, Sri City, Chittoor


Set-2.

Name of the Exam: Circuits and Networks

Duration:


Max. Marks: 17

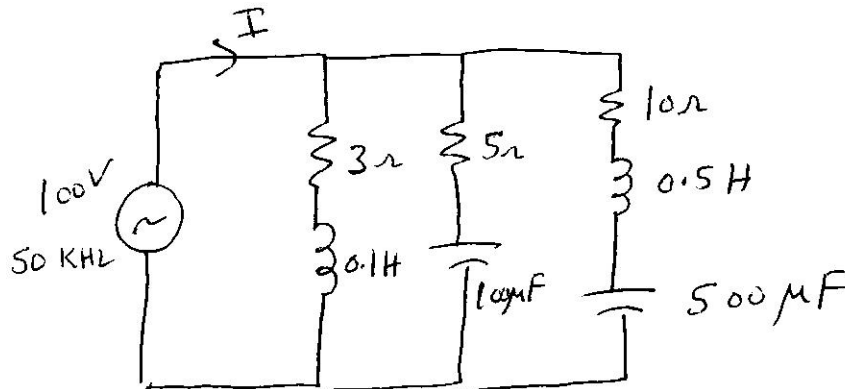1. for the given circuit, find I in rectangular & polar form.




(5 Marks)

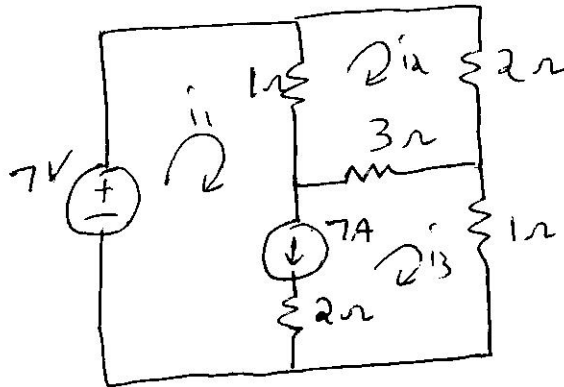2. for the given circuit, write the equations using mesh analysis. If $i_3 = 2A$, find i_1 & i_2 .



(4 Marks)

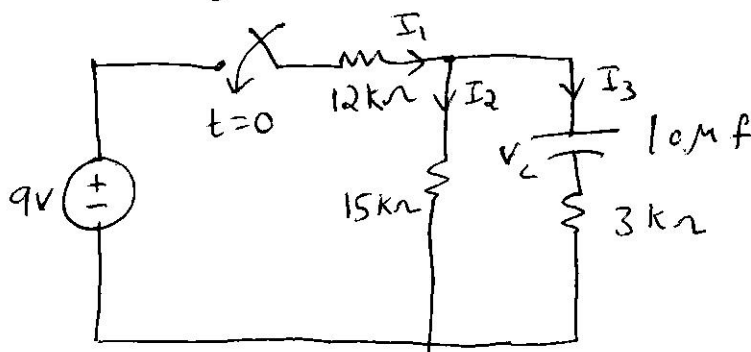3. for the given circuit, find I_1, I_2, I_3 & V_C at $t=0$



4) find $i(t)$ for $t > 0$. switch open at $t = 0$

