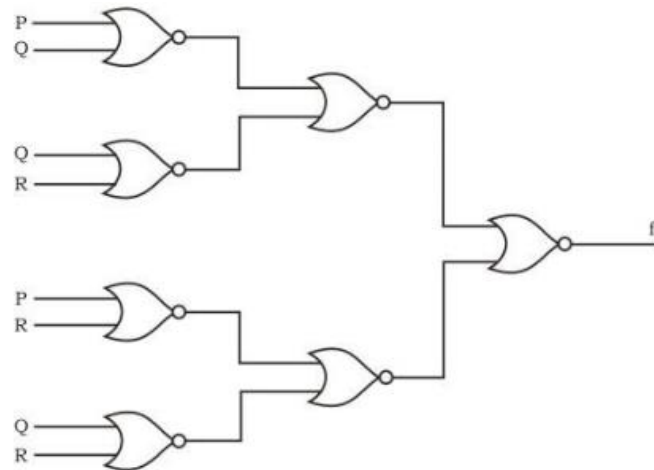


Indian Institute of Information Technology, Sri City, Chittoor

Name of the Exam: Digital Design SET2 Duration: 60+30 mins (for uploading) Max. Marks: 18

Question 1 to 4: 4 marks each, Question 5: 2 marks

- For the given circuit diagram (NOR gates), applying Boolean algebra find the minimized expression for output F=



- Design a Full subtractor using two half subtractors (include truth table, K-maps, logic expression and diagram)
- Write the truth table of 8x3 encoder by encoding single bit 0. Include logic expression and circuit diagram. Represent inputs D0 to D7, and outputs X, Y and Z.
- 1) Simplify into SOP using K-maps and draw the logic diagram for simplified expression
 i) $F(a,b,c,d)=\sum(0,1,2,5,8,9,10)$ ii) $F(a,b,c,d)=\sum(0,2,4,5,6,7,8,10,13,15)$
- Write the complete truth table of BCD to 7 segment decoder. (K-maps and circuit diagram not required)

